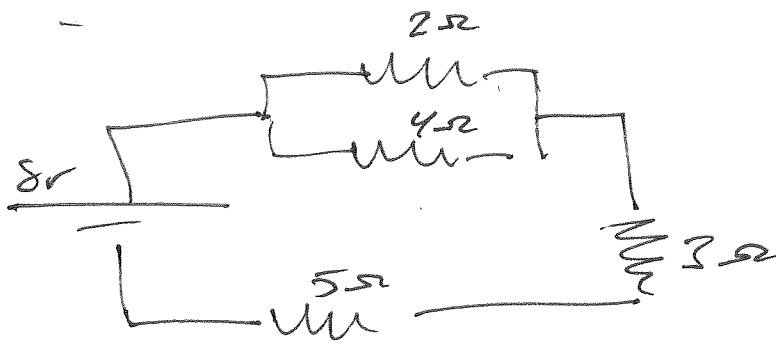


①



$$\textcircled{1} \quad \frac{1}{2} + \frac{1}{4} = \frac{1}{R_{\text{net}}} \therefore R_{\text{net}} = 1.33 \Omega$$

$$\textcircled{2} \quad R_{\text{total}} = 1.33 \Omega + 3 \Omega + 5 \Omega = 9.33 \Omega$$

$$\textcircled{3} \quad \text{total current } I = \frac{V}{R} = \frac{8V}{9.33 \Omega} = 0.857 \text{ amps}$$

$$\textcircled{4} \quad (0.857 \text{ A})(5 \Omega) = 4.28 \text{ volts}$$


$$(0.857 \text{ A})(3 \Omega) = 2.57 \text{ volts}$$

$$\textcircled{5} \quad \boxed{8V - 4.28V - 2.57 \text{ volts}} = 1.15 \text{ volts across } 2 \Omega + 4 \Omega \text{ resistors}$$

$$\text{Voltage across } 4 \Omega = 1.15 \text{ volts}$$

$$\text{Current through } 4 \Omega = \frac{1.15V}{4 \Omega} = 0.287 \text{ amps}$$

(2)

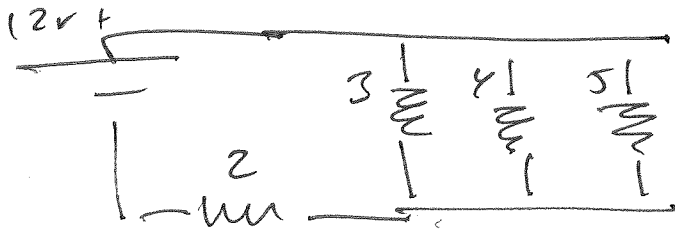

$$(1) \quad \frac{1}{3} + \frac{1}{4} + \frac{1}{5} = \frac{1}{R_{net}} = \frac{20}{60} + \frac{15}{60} + \frac{12}{60} = \frac{47}{60} = \frac{1}{R_{net}}$$

$$(2) \therefore R_{net} = \frac{60}{47} \approx 1.3 \Omega \text{ total}$$

$$(3) \quad \frac{12V}{(1.3 \Omega + 2 \Omega)} = \frac{12V}{3.3 \Omega} = 3.64 \text{ amps total}$$


$$(4) \quad \text{Voltage across } 2 \Omega \text{ resistor is } (3.64 \text{ amp}) (2 \Omega) = 7.2 \text{ volts}$$

$$\therefore \text{Therefore, } 12V - 7.2 \text{ volts} = \boxed{4.8 \text{ volts across}}$$

the 3, 4 and 5  $\Omega$  resistors.

$$\text{So... } V = IR \quad \frac{V}{R} = I \quad \frac{4.8V}{4 \Omega} = \boxed{1.17 \text{ amps}}$$

(3)

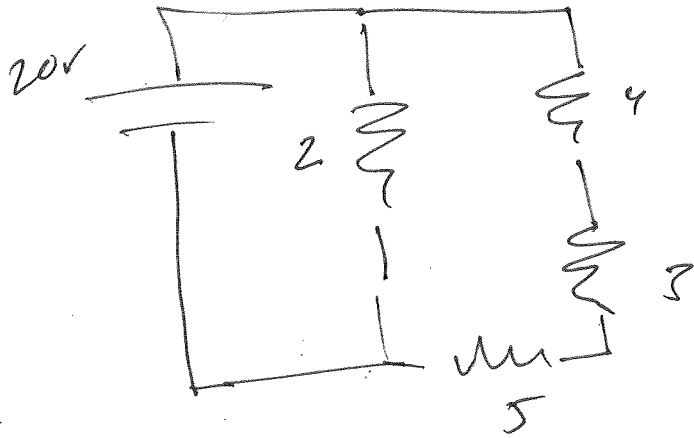


note: the 4, 3 and 5  $\Omega$  resistors are all in series, and that entire branch "sees" 20 volts

$$(1) 4 + 3 + 5 = 12 \Omega \text{ total}$$

$$\therefore \frac{20V}{12\Omega} = \boxed{1.66 \text{ amps}}$$

$$(2) V = IR = (1.66A)(4\Omega) = \boxed{6.67 \text{ volts}}$$

(4)

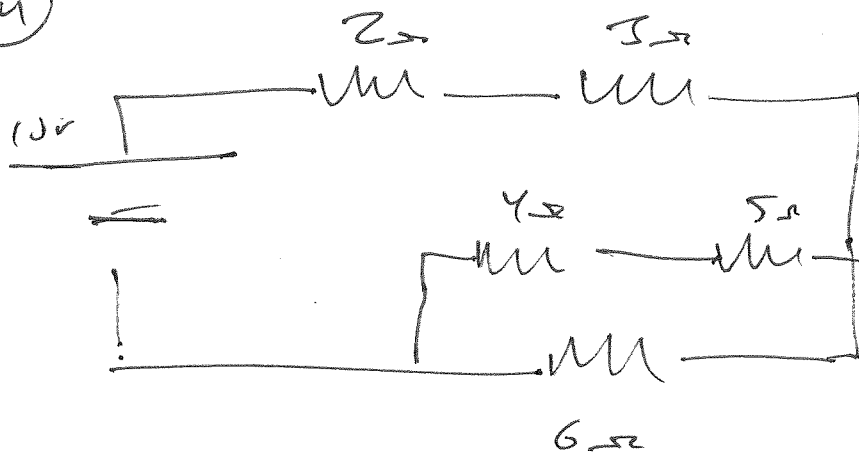

(1)  $2\Omega + 3\Omega = 5\Omega$

$4\Omega + 5\Omega = 9\Omega$

$\frac{1}{9} + \frac{1}{6} = \frac{2}{18} + \frac{3}{18} = \frac{5}{18} = \frac{1}{R_{net}} \therefore R_{net} = 3.6\Omega$

(2)  $2\Omega + 3\Omega + 3.6\Omega = 8.6\Omega$  total

(3)  $V = IR \quad \frac{V}{R} = I = \frac{10V}{8.6\Omega} = 1.16 \text{ amps}$  total

(4)  $(1.16A)(2\Omega) = 2.32 \text{ volts}$

$(1.16A)(3\Omega) = 3.48 \text{ volts}$

5.8 volts across  $2\Omega + 3\Omega$

so  $10V - 5.8V = 4.2 \text{ volts}$

across the  $4\Omega + 5\Omega$  in series.

$V = IR \quad \frac{V}{R} = I \quad \frac{4.2V}{9\Omega} = 0.46 \text{ amps through } 4\Omega$

$\therefore \text{th. } V = IR = (0.46A)(4\Omega) = 1.84V$